

**Department of Physics Nirmala College Muvattupuzha**  
**Laboratory Manual for BSc. Physics Model 2 (Semester 2)**

**Applied electronics**

**2017-2020**

**Compiled and Edited**

**by**

**Dr. Aloysius Sabu N**

**Associate Professor of Physics**

## 1. Characteristics of Junction Field Effect Transistor (JFET)

### Aim:

To study the Drain and Transfer Characteristics of a Junction Field Effect Transistor (JFET).

### Components:

JFET (BFW10), Bread board, Regulated Power supply (0 - 2 V) and (0 - 12 V), Ammeters (0 - 20 mA), Voltmeter  $V_1$  (0 - 2V), Voltmeter  $V_2$ , (0 - 10V), Connecting wires (Single Strand)

### Theory and Operation:

1. Drain characteristics are obtained between the drain to source voltage ( $V_{DS}$ ) and drain current ( $I_D$ ) taking gate to source voltage ( $V_{GS}$ ) as the constant parameter.
2. Transfer characteristics are obtained between the gate to source voltage ( $V_{GS}$ ) and drain current ( $I_D$ ) taking drain to source voltage ( $V_{DS}$ ) as the constant parameter.

### FET Parameters

1. **Drain Resistance ( $r_d$ ):** It is given by the relation of small change in drain to source voltage ( $\Delta V_{DS}$ ) to the corresponding change in Drain Current ( $\Delta I_D$ ) for a constant gate to source voltage ( $\Delta V_{GS}$ ), when the JFET is operating in pinch-off region.

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \text{ at a constant } V_{GS} \text{ (from drain characteristics)}$$

2. **Trans Conductance ( $g_m$ ):** Ratio of small change in drain current ( $\Delta I_D$ ) to the corresponding change in gate to source voltage ( $\Delta V_{GS}$ ) for a constant  $V_{DS}$ .

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \text{ at constant } V_{DS} \text{ (from transfer characteristics).}$$


The value of  $g_m$  is expressed in mho's ( $\Omega$ ) or Siemens (s).


3. **Amplification factor ( $\mu$ ):** It is given by the ratio of small change in drain to source voltage ( $\Delta V_{DS}$ ) to the corresponding change in gate to source voltage ( $\Delta V_{GS}$ ) for a constant drain current ( $I_D$ ).

$$\mu = \left( \frac{\Delta V_{DS}}{\Delta I_D} \right) \times \left( \frac{\Delta I_D}{\Delta V_{GS}} \right) = \frac{\Delta V_{DS}}{\Delta V_{GS}}$$

$$\text{ie. } \mu = r_d \times g_m$$

### Pin assignment of FET:

 

 **Circuit Diagram:****Procedure:****Drain Characteristics:**

1. Connect the circuit as shown in the figure 1.
2. Keep  $V_{GS} = 0V$  by varying  $V_{GG}$ .
3. Varying  $V_{DD}$  gradually in steps of  $1V$  up to  $10V$  note down drain current  $I_D$  and drain to source voltage ( $V_{DS}$ ).
4. Repeat above procedure for  $V_{GS} = -0.4, -0.8, -1.2$  and  $-1.6 V$


**Transfer Characteristics:**

1. Connect the circuit as shown in the figure 1.
2. Set voltage  $V_{DS} = 4V/8V$
3. Varying  $V_{DS}$  in steps of  $0.5V$  until the current  $I_D$  reduces to minimum value.
4. Varying  $V_{GG}$  gradually, note down both drain current  $I_D$  and gate-source voltage ( $V_{GS}$ ).
5. Repeat above procedure (step 3) for  $V_{DS} = 4V/ 8V$

**Observations:**

Drain Characteristics						
$V_{DS}$ (Volts)	$V_{GS} = 0V$		$V_{GS} = -0.4V$		$V_{GS} = -0.8V$	
	$V_{DS}$ (Volts)	$I_D$ (mA)	$V_{DS}$ (Volts)	$I_D$ (mA)	$V_{DS}$ (Volts)	$I_D$ (mA)
0						
2						
4						
6						
8						
10						

Transfer Characteristics			
$V_{DS} = 4V$		$V_{DS} = 8V$	
$V_{GS}$ (Volts)	$I_D$ (mA)	$V_{GS}$ (Volts)	$I_D$ (mA)
0			
0.5			
1.0			
1.5			

 **Graph:**

1. Plot the drain characteristics by taking  $V_{DS}$  on X-axis and  $I_D$  on Y-axis at a constant  $V_{GS}$ .
2. Plot the transfer characteristics by taking  $V_{GS}$  on X-axis and taking  $I_D$  on Y-axis at constant  $V_{DS}$ .

**Calculations from Graph:****1. Drain Resistance ( $r_d$ ):**

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \text{ at a constant } V_{GS} \text{ (from drain characteristics)}$$

**2. Trans Conductance ( $g_m$ ):**

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \text{ at constant } V_{DS} \text{ (from transfer characteristics).}$$

The value of  $g_m$  is expressed in mho's ( $\Omega$ ) or Siemens (s).

**3. Amplification factor ( $\mu$ ):** It is given by the ratio of small change in drain to source voltage ( $\Delta V_{DS}$ ) to the corresponding change in gate to source voltage ( $\Delta V_{GS}$ ) for a constant drain current ( $I_D$ ).

$$\mu = \left( \frac{\Delta V_{DS}}{\Delta I_D} \right) \times \left( \frac{\Delta I_D}{\Delta V_{GS}} \right) = \frac{\Delta V_{DS}}{\Delta V_{GS}}$$

$$\text{ie. } \mu = r_d \times g_m$$

**Result:** Drain and Transfer characteristics of a FET are studied.

**Outcomes:** Students are able to

1. Analyze the Drain and transfer characteristics of FET in Common Source configuration.
2. Calculate the parameters transconductance ( $g_m$ ), drain resistance ( $r_d$ ) and amplification factor ( $\mu$ ).

## 2. Characteristics of Uni-Junction Transistor (UJT)


### Aim:

To study and plot the characteristics of UJT


**Components:** UJT 2N 2646, Resistors (1 K ohm), Bread board, Regulated Power supply (0 - 2 V) and (0 - 12 V), Ammeters (0 - 20 mA), Voltmeter (0 - 2V), Voltmeter (0 - 10V), Connecting wires (Single Strand)
 
### Pin assignment of UJT:

The UJT- junction is a 3 - terminal solid-state device (emitter and the two bases)




### Circuit Diagram:

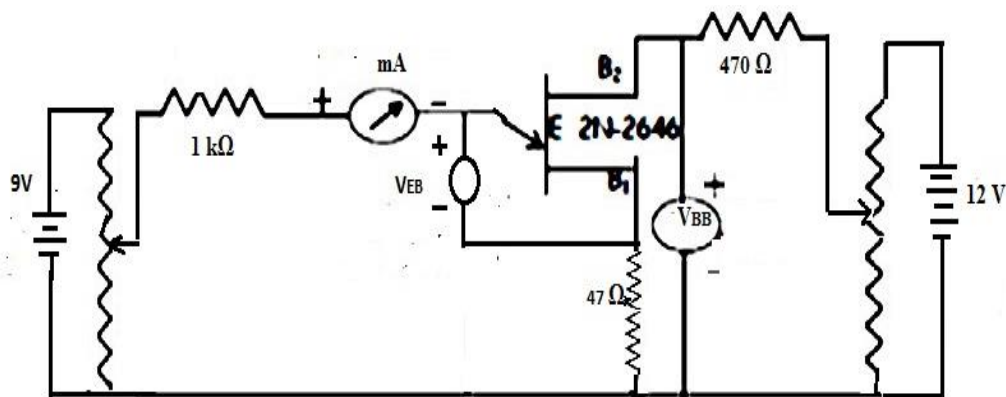
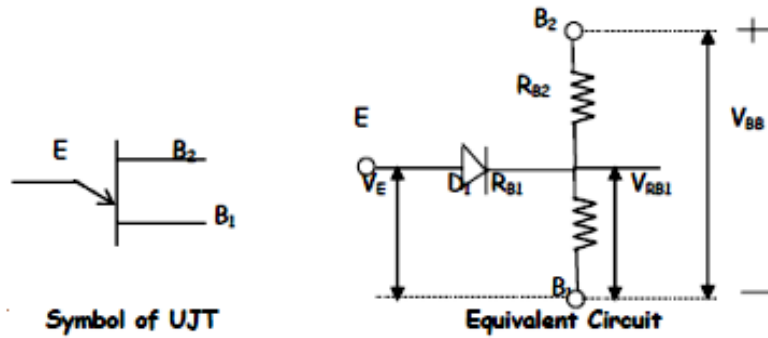
### Operation:

. The simplified equivalent circuit is shown below:



### Referring to equivalent circuit:

1. When no voltage is applied between  $B_1$  and  $B_2$  with emitter open, the inter base resistance is given by  $R_{BB} = R_{B1} + R_{B2}$ .
2. When a voltage  $V_{BB}$  is applied between  $B_1$  and  $B_2$  with emitter open, voltage will divide up across  $R_{B1}$  and  $R_{B2}$ .


$$V_{R_{B1}} = \frac{R_{B1}}{R_{B1} + R_{B2}} \times V_{BB}$$

$$\frac{V_{R_{B1}}}{V_{BB}} = \frac{R_{B1}}{R_{B1} + R_{B2}} \times V_{BB}$$

$$V_{R_{B1}} = \eta V_{BB},$$

where the intrinsic stand-off ratio
 
$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$



The typical value of  $\eta$  ranges from 0.56 to 0.75.

The potential drop  $\eta V_{BB}$  across  $R_{B1}$  reverse biases the diode thereby dropping the emitter current to zero. Here, up to the peak point, the diode is reverse biased and hence, the region to the left of the peak point is called cut-off region. When emitter voltage  $V_E$  equals the peak voltage  $V_P = \eta V_{BB} + V_D$ , the diode starts conducting and holes are injected into n-layer. Hence, resistance decreases thereby decreasing  $V_E$  for the increase in  $I_E$ . So there is a negative resistance region from peak point P to valley point V.

After the valley point, the device is driven into saturation and behaves like a conventional forward biased PN-junction diode. The region to the right of the valley point is called saturation region.

In the valley point, the resistance changes from negative to positive. The resistance remains positive in the saturation region.

### Procedure:

1. Connect the circuit as shown in the circuit diagram.
2. Set output voltage  $V_{BB} = 8V$  by varying  $V_{BB}$ .
3. Varying  $V_{EE}$  gradually, note down both emitter current  $I_E$  and emitter voltage ( $V_E$ ).
4. Step size is not fixed because of non linear curve. Initially Vary  $V_{EE}$  in steps of 1V. Current  $I_E$  remains zero. As voltage is varied further, current starts increasing while voltage  $V_E$  drops. Note down the readings  $V_E$  and  $I_E$ .
5. Repeat above procedure (step 3) for  $V_{BB} = 10V$ .
6. Plot the tabulated readings on a graph sheet with  $I_E$  on X-axis and  $V_E$  on Y-axis.

**Observations:**

$V_{BB} = 8V$		$V_{BB} = 10V$	
$I_E(\text{mA})$	$V_E(\text{V})$	$I_E(\text{mA})$	$V_E(\text{V})$

**Inference:**

1. There is a negative resistance region from peak point to valley point.
2. Increase in  $V_{BB}$  increases the value of peak and valley voltages.

**Result:**

The emitter characteristics of UJT are studied.

- a. Peak Voltage,  $V_p$  \_\_\_\_\_ Volts.
- b. Valley Voltage,  $V_v$  \_\_\_\_\_ Volts.
- c. Valley Current,  $I_v$  \_\_\_\_\_ mA.
- d. Negative Resistance \_\_\_\_\_ Ohms
- e. Intrinsic stand-off ratio  $\eta$  -----


**Outcome:** Students are able to obtain the Emitter characteristics of UJT  
Students are able to appreciate the invention of UJT

### 3. V-I Characteristics of Silicon controlled rectifier (SCR)


**Aim:** To draw the V-I Characteristics of Silicon controlled rectifier.

**Apparatus:** SCR (2P4M), Regulated Power Supplies (0-2V) and (0-12V), Resistors 10k $\Omega$ , 1k $\Omega$ , Ammeter (0-20) mA, Voltmeter (0-12V), Breadboard and Connecting Wires.

**Circuit Diagram:**

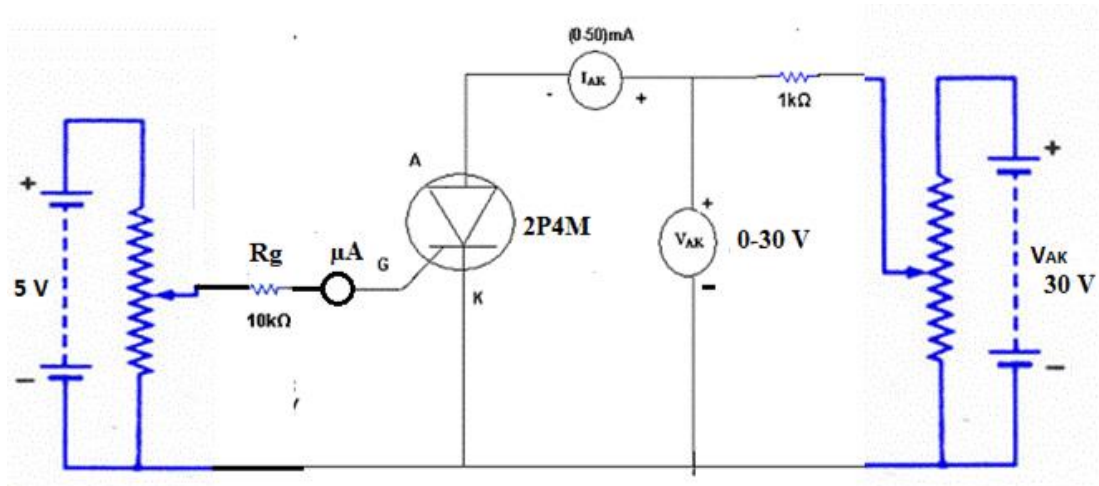

**Symbol of SCR**

 

**Theory:**

It is a four layer semiconductor device being alternate of P-type and N-type silicon. It consists of 3 junctions  $J_1$ ,  $J_2$ ,  $J_3$  the  $J_1$  and  $J_3$  operate in forward direction and  $J_2$  operates in reverse direction and three terminals called anode A, cathode K, and a gate G. The operation of SCR can be studied when the gate is open and when the gate is positive with respect to cathode.



When gate is open, no voltage is applied at the gate due to reverse bias of the junction  $J_2$  no current flows through  $R_2$  and hence SCR is at cut off. When anode voltage is increased  $J_2$  tends to breakdown.

When the gate positive, with respect to cathode  $J_3$  junction is forward biased and  $J_2$  is reverse biased. Electrons from N-type material move across junction  $J_3$  towards gate while holes from P-type material moves across junction  $J_3$  towards cathode. So gate current starts flowing, anode current increases in extremely small current, junction  $J_2$  break down and SCR conducts heavily.

When gate is open the break-over voltage is determined on the minimum forward voltage at which SCR conducts heavily. Now most of the supply voltage appears across the load resistance. The holding current is the maximum anode current gate being open, when break over occurs.

### **Procedure:**


1. Connections are made as per circuit diagram.
2. Keep the gate supply voltage at some constant value
3. Vary the anode to cathode supply voltage and note down the readings of voltmeter and ammeter. Keep the gate voltage at standard value.
4. A graph is drawn between  $V_{AK}$  and  $I_{AK}$ .

### **Observation:**

<b><math>I_g =</math> ( <math>\mu A</math> )</b>	
<b><math>V_{AK}(V)</math></b>	<b><math>I_{AK} (mA)</math></b>

<b><math>I_g =</math> ( <math>\mu A</math> )</b>	
<b><math>V_{AK}(V)</math></b>	<b><math>I_{AK} ( mA)</math></b>

### **Model Wave form:**

 

**Result:** SCR Characteristics are observed.





**OUTCOME:** Students are able to obtain the Emitter characteristics of SCR

#### 4. Characteristics of a DIAC

**AIM:** To plot the VI characteristics of a DIAC

**APPARATUS REQUIRED:** DIAC (DB 32), power supply (50 V), DMM, Bread board  
Connecting wires (Single Strand)

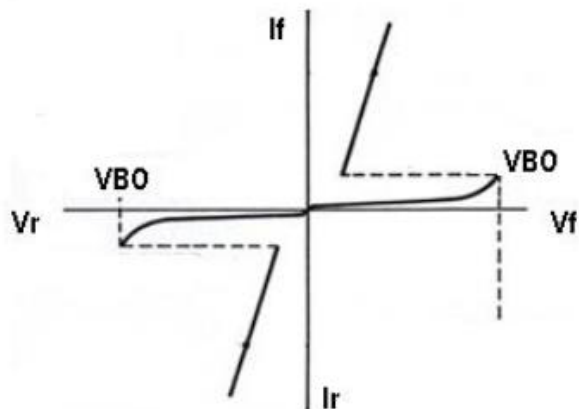  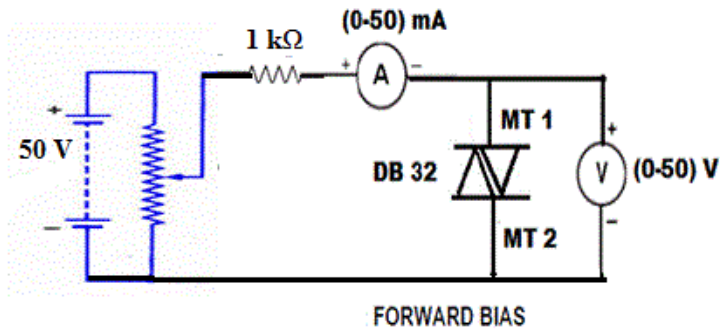**THEORY:** DIAC is a diode that can work on AC. The DIAC has symmetrical breakdown characteristics. The leads are interchangeable. It turns on around 32V. While conducting, it acts like a low resistance with a drop of around 3V. When not conducting, it acts like an open switch.



### PROCEDURE:

1. Connect the circuit as per the circuit diagram.
2. Change the voltage in steps till 32V and observe Voltmeter reading and Ammeter reading. Note the start of break overvoltage. Observe the conduction of DIAC..
3. Now change the DIAC direction and vary the voltage insteps in the negative direction till - 32V and Observe Voltmeter reading and Ammeter reading. Note the start of break overvoltage. Observe the conduction of DIAC.

.4. The characteristics are tabulated and plotted.

OBSERVATIONS:

Forward Characteristics		Reverse Characteristics	
$V_f$ (V)	$I_f$ (mA)	$V_r$ (V)	$I_r$ (mA)

**RESULT:** The VI characteristics of a DIAC have been plotted.

**OUTCOME:**


- Students acquire skill in connecting components using breadboard and connecting wires to form circuit.
- They become able to determine the Emitter characteristics of SCR

## 5. UJT as a Relaxation Oscillator


**Aim:** To Study the operation of UJT as a Relaxation Oscillator

**Apparatus:** UJT (2N2646), CRO (0 – 20 MHz (Dual channel), Function generator 1Hz – 1 MHz, Capacitor (0.1 $\mu$ F), Resistors (100  $\Omega$ , 47  $\Omega$ , 10 k  $\Omega$ ), Bread board and connecting wires, Regulated Power supply 0-12V DC

**Circuit diagram:**

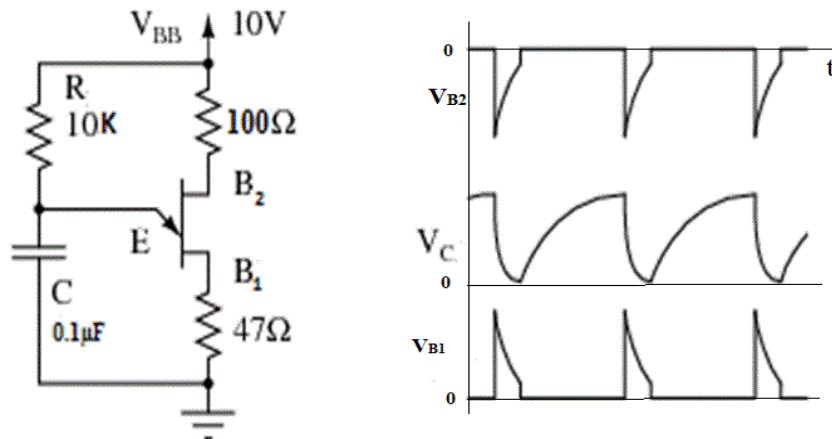

**Pin assignment of UJT:**

 

Viewing from the side of pins

**Frequency of oscillations:**

The time period and hence the frequency of the saw-tooth wave can be calculated as follows:

$$T = RC \log_e \left( \frac{1}{1-\eta} \right)$$

$$= 2.303RC \log_{10} \left( \frac{1}{1-\eta} \right)$$

If the discharge time of the capacitor is neglected, then  $t = T$ , the period of the wave. Therefore, frequency of oscillations of saw-tooth wave,

$$f = \frac{1}{T} = \frac{1}{2.303RC \log_{10} \left( \frac{1}{1-\eta} \right)}$$

**Design**

From the data sheet of UJT 2N2646,

$\eta = 0.56$  to  $0.75$ , Typical value of  $\eta = 0.6$ ,  $V_V = 1.5$  V,  $I_P = 5$   $\mu$ A and  $I_V = 4$  mA

$V_P = \eta V_{BB} + V_D = (0.6 \times 9) + 0.7 = 6.1$  V

$$R_{max} = \frac{V_{BB} - V_P}{I_P} = \frac{9 - 6.1}{5 \mu A} = \frac{2.9}{5} M\Omega = 0.58 M\Omega$$

$$R_{min} = \frac{V_{BB} - V_V}{I_V} = \frac{9 - 1.5}{4 mA} = \frac{7.5}{45} k\Omega = 1.875 k\Omega$$

Taking geometric mean,

$$R = \sqrt{R_{max} \times R_{min}} = \sqrt{(0.58M\Omega \times 1.875 k\Omega)} = 32.76 k\Omega$$

Select,  $R = 33 k\Omega$ . For convenience select  $R = 10 k\Omega$

Let the required frequency be 1 kHz, then  $T = 1/f = 10^{-3}s$ .

$$T = RC \log_e \left( \frac{1}{1-\eta} \right)$$

$$10^{-3}s = 10 \times 10^3 \times C \log_e \left( \frac{1}{1-0.6} \right)$$

$$C = \frac{10^{-7}}{\log_e \left( \frac{1}{1-0.6} \right)} = \frac{10^{-7}}{0.9163} = 0.1 \mu F$$

### Procedure:

1. Connect the circuit as shown in figure.
2. Apply 10 V DC power supply to the circuit.
3. Observe the output waveform on the CRO at B1, B2 and  $V_O$  and Plot the graphs
4. Vary the time constant (RC) by varying capacitor (C) or potentiometer (R) and observe the variations in the output pulses on the CRO at B1, B2 and  $V_O$ .

### Result:

UJT relaxation oscillator is constructed and output waveforms are obtained.

Frequency of oscillations = -----Hz.

### Outcome:

- After finishing this experiment students are able to understand the operation of UJT as a relaxation oscillator.
- Students become able to design a relaxation oscillator

## 6. JFET common source amplifier


### Aim:

To study the JFET common source amplifier and find its cut off frequencies and Bandwidth.

**Components:** JFET BFW 10, Resistor 2.7K $\Omega$ , 1.0 K $\Omega$ , 100 K $\Omega$ , Capacitor 10 $\mu$ F, 22 $\mu$ F, Bread Board, power supply, Function Generator, Connecting Wires.

**Theory:**

The JFET is a unipolar voltage controlled device. The drain current is controlled by the voltage applied at the gate. In the circuit shown self bias maintains drain current and mutual conductance  $g_m$  relatively constant. Constant  $g_m$  results a constant voltage gain. The reverse biased junction provides high input impedance.

 **Circuit Diagram:****Procedure:**


1. Connect the circuit as shown in the circuit diagram.
2. Set source voltage  $V_s = 50\text{mV}$  (say) at 1 KHz frequency using the function generator.
3. Keeping input voltage constant vary the frequency from 50 Hz to 1 MHz in regular steps and note down the corresponding output voltage.
4. Plot the graph: gain (dB) versus Frequency on a semi log graph sheet.
5. Calculate the bandwidth from the graph.
6. Calculate all the parameters at mid band frequencies (i.e. at 1 KHz).
7. To calculate voltage gain

$$\text{Gain } A = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{V_o}{V_i}$$

$$\text{Gain in (dB)} = 20 \log (V_o/V_i)$$

**Expected waveform:**

In the usual application, mid band frequency range are defined as those frequencies at which the response has fallen to 3dB below the maximum gain ( $|A|_{\text{max}}$ ). These are shown as  $f_L$  and  $f_H$  and are called as the 3dB frequencies are simply the lower and higher cut off frequencies respectively. The difference between higher cut off and lower cut off frequency is referred to as bandwidth ( $f_H - f_L$ ).

 

### Observation tables:

$V_i = 50\text{mV}$

Frequency	$V_o$ (volts)	Gain= $V_o/V_s$	Gain(dB)= $20 \log(V_o/V_s)$

Lower cut-off frequency ( $f_L$ ) =

Upper cut-off frequency ( $f_H$ ) =

Bandwidth  $\beta = f_H - f_L =$

### Result:

JFET common source amplifier is studied and its cut off frequencies and Bandwidth is found.

### Outcome:

Students are able to determine the bandwidth of common source JFET amplifier.


## 7. V-I Characteristic of TRIAC

**Aim:** - To study V-I characteristic of TRIAC.

**Apparatus:** - TRIAC BT 136, Circuit board 0-300V high voltage supply, 0-30V low voltage supply, Ammeter (0-10mA, 0-1A), voltmeter (0-250V), Resistor  $10\text{K}\Omega$ ,  $1.5\text{K}\Omega$  connecting wires

**Circuit Diagram**



 

**Theory:** A TRIAC is a device which can be turned on through the gate pulse for both positive and negative values of  $V_{AK}$  and turned off using power circuit i.e., turn on is controlled but turn off is uncontrolled in a TRIAC. The voltage at which the TRIAC gets into conduction state is called forward breakover voltage ( $V_{BO}$ ) for positive voltages and reverse break over voltage ( $V_{BR}$ ) for negative voltages. If the gate current is increased then the forward break over and reverse break over voltages will be reduced. The current at which the TRIAC turns on is called latching current ( $I_L$ ). Once the TRIAC is turned on, no need of the gate pulse i.e., gate pulse can be removed once the device is turned on. The minimum current required for the device to keep the thyristor on is holding current ( $I_H$ ). The ratio of latching to holding currents will be 3-5. When the gate current is increased, the break over voltage values will be reduced.

### Procedure:

#### Mode 1

1. Connect the circuit as per the connection diagram.
2. Keep the gate current a fixed value ( $I_{g1}$ ).
3. By varying the anode to cathode voltage note the voltage ( $V_{ak}$ ) and current ( $I_a$ ).
4. Note the forward break over voltage ( $V_{BO}$ ), latching current ( $I_L$ ) and holding current ( $I_H$ ).
5. Change the gate current value ( $I_{g2}$ ,  $I_{g3}$ ) and repeat steps 3 and 4.

6. Plot the graph between  $V_{AK}$  and  $I_A$ , denoting  $I_L$ ,  $I_H$ , and  $V_{BO}$ 's.


**Mode 2**

Connect are made as shown in circuit diagram. 2 Step no. S 2, 3, 4,5 and 6 are to be repeated as in mode 1.

**Precautions:**

1. While changing the gate current, first make the  $V_{AK}$  equal to zero and then vary  $I_g$ .

**Model Graph:**

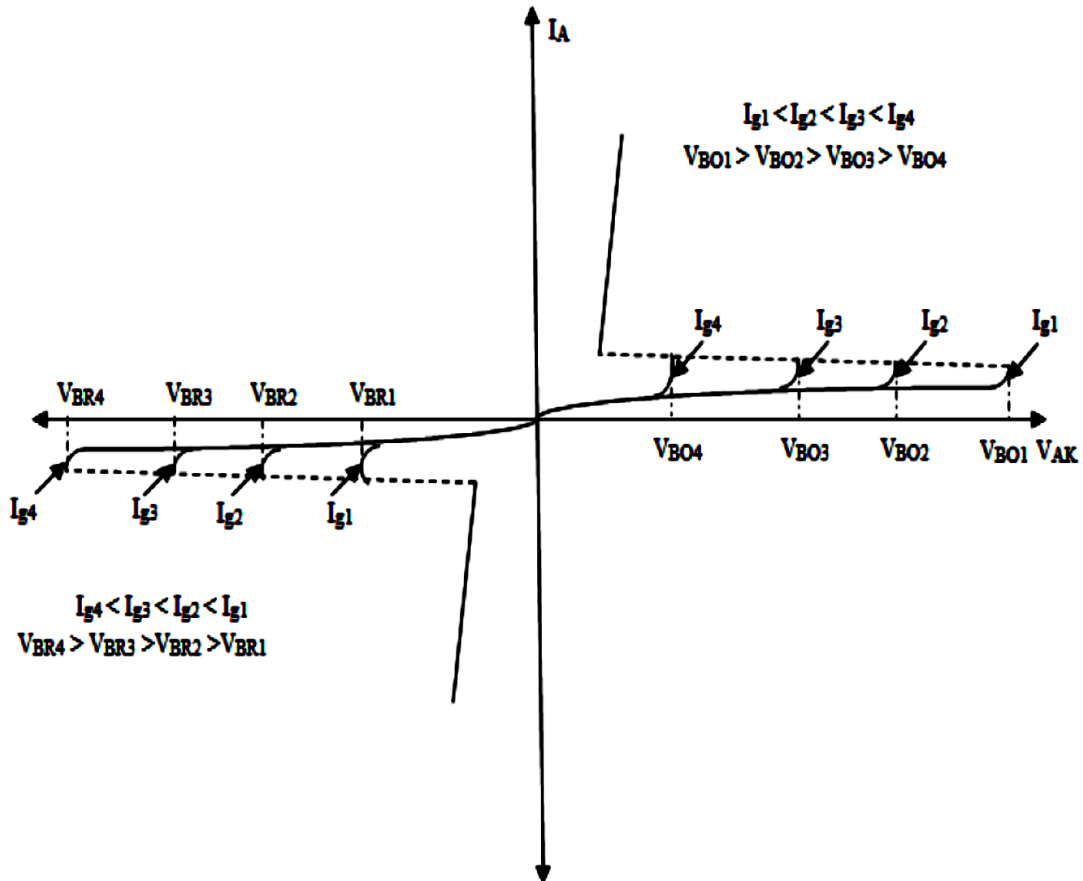

$I_g = \quad (\mu A)$		$I_g = \quad (\mu A)$	
$V_{AK}(V)$	$I_{AK} (mA)$	$V_{AK}(V)$	$I_{AK} (mA)$

<b>I<sub>g</sub> = (μA)</b>		<b>I<sub>g</sub> = (μA)</b>	

**Result:**

Characteristics of TRIAC are studied for two different triggering currents.

**Outcome**

Students are able to understand the working principle of a TRIAC